

uartICE40 — Asynchronous receiver/transmitter for iCE40 FPGAs

Baard Nossum

July 20, 2016

Contents

Contents	i
1 Introduction	1
1.1 Features	1
1.2 Project scope and documentation	1
2 Top level	2
3 Transmit module	3
3.1 High level implementation	3
3.2 Low level implementation	4
4 Receive module	7
4.1 High level implementation	7
4.2 Low level implementation	10
5 The dividers	11
5.1 High level implementation	11
5.2 Low level implementation	12

6	All together	14
6.1	High level implementation	14
6.2	Low level implementation	14
7	Testbench	15
7.1	What do we test?	15
7.2	Test bench proper	15
7.3	Use of the test bench	19
8	ICEstick	20
8.1	Compilation results	22
8.1.1	Synplify, low level	22
8.1.2	Synplify, high level	23
9	Conclusion	24

Introduction

1.1 Features

- Specifically written for iCE40
- Easy to use
- Small footprint, 32 (default) or 34 logicCells
- Format is hardcoded: 8 data bits, no parity, one stop bit (8N1)
- Samples RX pin 8 (default) or 16 times per bit period

A note on nomenclature

In practical terms, the `usart`¹ is nearly always used asynchronously, with 8 data bits. There are still applications that relies on 1 or 2 stop bits, and odd or even parity, but a large majority of applications uses 1 stop bit, no parity. The module described in this paper should perhaps be called an `art` (asynchronous receiver/transmitter), but I bow to conventions and call the module an “`uart`”.

1.2 Project scope and documentation

Two verilog source code files, `uartICE40` and `uartICE40hl` are the results of this project. The rest of the files are just there to verify that those two files are correct. The files `uartICE40` and `uartICE40hl` should be functionally identical. While `uartICE40` is written using primitives of the iCE40 architecture, the corresponding “high-level” `uartICE40hl` is synthesized from standard Verilog. Motivation for two different implementations is simply that it is cumbersome to understand a low level implementation that relies on explicitly instantiated LUTs. FPGA projects often have many dependencies, and files. Users of the two files above will need to move the files to relevant locations,

Documentation and code is generated using `noweb`.² It is a paradox that documentation of such a small and easy module extends to 24 pages.

¹`usart`: Universal, synchronous/asynchronous receiver transmitter. This implies that it can be used synchronous with an external clock. “universal” denotes that one can select the number of data bits and stop bits, and whether (odd or even) parity is to be used or not.

²For those unfamiliar with `noweb` - it is a tool that allow writing of documentation and of code in the same textfile. A definite advantage is that the code that is documented is indeed the code that is generated.

Top level

uartICE40 has the following interface:

2a `<module head 2a>≡` (14)

```
module uartICE40
  # (parameter SUBDIV16 = 0, // Examine rx line 16 or 8 times per bit
    ADJUSTSAMPLEPOINT = 0 // Set to 1 when bitrate*8/clock < 2 (SUBDIV16 = 0),
  ) ( // or bitrate*16/clock < 2 (for SUBDIV16 = 1).
    input      clk, // System clock
    input      bitxclk, // High 1 clock cycle 8 or 16 times per bit
    input      load, // Time to transmit a byte. Load transmit buffer
    input [7:0] d, // Byte to load into transmit buffer
    input      rxpin, // Connect to receive pin of uart
    output     txpin, // Connect to INVERTED transmit pin of uart
    output     txbusy, // Status of transmit. When high do not load
    output     bytercvd, // Status receive. True 1 clock cycle only
    output [1:0] rxst, // Testbench need access to receive state machine
    output [7:0] q // Received byte from serial receive/byte buffer
  );
```

uartICE40 top module instantiates three submodules. It does not contain any code itself. To limit typing, I use the verilog mode of emacs. Verilog source files are expanded so that the source code is usable to those programmers that do not use emacs.

2b `<module body 2b>≡` (14)

```
/*AUTOWIRE*/
uarttx_m uarttx_i (*AUTOINST*);
uartrx_m uartrx_i (*AUTOINST*);
rxtxdiv_m #( .ADJUSTSAMPLEPOINT(ADJUSTSAMPLEPOINT),
             .SUBDIV16(SUBDIV16) )
rxtxdiv_i
(*AUTOINST*);
endmodule
```

To use uartICE40 in a project, only the interface above really need to be respected. Unless you want to know how it's innards work, you can stop reading now.

Transmit module

A uart transmitter is very simple. Basically we load a shift register with the byte to transfer, and shift the byte out one and one bit. Before shifting out the first (lsb) data bit, we must shift out the start bit. After the byte has been shifted out, we must shift out the stop bit. A status output tells if the transmit module is busy.

3.1 High level implementation

The interface to the transmit module has the system clock as input. When data is to be loaded, it is given to this module on the 8-bit `d` input, qualified by `load`. This module should shift each `txce` clock cycle. `txce` is logically or'ed with `load`. The shift register is 10 bits: The transmit shift register only changes when we load data, or when `txce` is active. When this happens, we do the following:

```

3  <hl uarttx module 3>≡ (14a)
    module uarttx_m
      (input      clk,load,load0Rtxce,
       input [7:0] d,
       output reg txpin, txbusy
      );
      reg [9:0] a;
      always @(posedge clk)
        if ( load0Rtxce ) begin
          a[9:0] <= load ? {1'b0,d,1'b0} : {1'b0,a[9:1]};
          txbusy <= load | |a[9:1];
          txpin  <= (load & txpin) | (!load & |a[9:1] & a[0]);
        end
    endmodule

```

- iCE40 FPGAs starts up with all flip-flops (FF) cleared. At power-up, I want the uart to be inactive. The easiest way to do this is probably to *invert* the pin output. But then we must compensate by inverting the data byte during load.
- If the shift register is not completely empty, or if we are loading the shift register, the transmit module is busy.
- Loading of the shift register is asynchronous to shifting, a FF is used to synchronize the shift register to `txce`. This give the `txpin` output FF.

Synplify or yosys is not able to understand that `txbusy` can be found out of the carry chain. This module is written this way to better explain the low level implementation in the next section.

3.2 Low level implementation

The transmit part in 12 LogicCells. txpin is to be connected to a pad with *inverted* output. This way uart transmit will go to inactive during power-up. The main idea here is to have a 10-bit shift register. When all bits are shifted out, a fact we find from the carry chain, transmission is done. We also need a FF to synchronize "load" with "txce".

In addition we need a FF to record that the shift register is busy. The shift register is busy from the clock cycle after it is loaded, until start of transmit of the stop bit. For continuous transfer, a microcontroller is expected to hook up ~txbusy as an interrupt source. A new byte must then be output in 7/8 bit times. An example: At 12 MHz clock, 115200 bps, a new byte must be written in at most 91 clock cycles to saturate the transmit path. The layout of the low-level implementation is shown in figure 3.1. In an ideal world, the high level description would map into this use of resources, but since the world is less than ideal, we must write it ourselves.

The module head is very similar to the high level implementation. When it comes to variables, a few more are needed:

```

4a  <ll uarttx module head 4a>≡ (14b)
    module uarttx_m
    (
        input      clk,load,load0Rtxce,
        input [7:0] d,
        output      txpin,
        output      txbusy
    );
    genvar      i;
    wire         c_txbusy,c_pp;
    wire [9:0]    c_a,a;
    wire [10:1]   cy;

```

The stop bit is set when we load, and cleared when we shift. We implement `ff <= load | ff*~txce`

```

4b  <ll uarttx module code 4b>≡ (14b) 4c▷
    SB_LUT4 #(.LUT_INIT(16'haaaa))
    ff_i(.O(c_a[9]), .I3(1'b0), .I2(1'b0), .I1(1'b0), .I0(load));
    SB_DFFE ff_r(.Q(a[9]), .C(clk), .E(load0Rtxce), .D(c_a[9]));

```

A generate statement takes care of the shift register with parallel load. Zerodetection takes place in the carry chain:

```

4c  <ll uarttx module code 4b>+≡ (14b) <4b 6a>
    generate
        for ( i = 0; i < 9; i = i + 1 ) begin : blk
            if ( i == 0 ) begin
                SB_LUT4 #(.LUT_INIT(16'h55cc))
                shcmb( .O(c_a[i]), .I3(load), .I2(1'b1), .I1(a[i+1]), .I0(1'b0));
                SB_CARRY shcy(.CO(cy[i+1]), .CI(1'b0), .I1(1'b1), .I0(a[i+1]));
            end else begin
                SB_LUT4 #(.LUT_INIT(16'h55cc))
                shcmb( .O(c_a[i]), .I3(load), .I2(1'b1), .I1(a[i+1]), .I0(d[i-1]));
                SB_CARRY shcy(.CO(cy[i+1]), .CI(cy[i]), .I1(1'b1), .I0(a[i+1]));
            end
            SB_DFFE r(.Q(a[i]), .C(clk), .E(load0Rtxce), .D(c_a[i]));
        end
    endgenerate

```

Figure 3.1: The transmit module in it's low-level version

Transmit is busy from the cycle after load, until the cycle where transmission of the stop bit starts. An implication is that the unit feeding the transmitter has a rather short window to write a new byte if continuous transmission is desired. $txbusy \leftarrow load \mid (\sim load \ \& \ a[9:1]) \mid (\sim load \& \sim txce \& txbusy)$ is implemented. Note that carry is transported unchanged across this LUT.

6a $\langle ll \text{ uarttx module code 4b} \rangle + \equiv$ (14b) $\triangleleft 4c \ 6b \triangleright$

```

SB_LUT4 #(.LUT_INIT(16'hffaa))
txbusy_i( .O(c_txbusy), .I3(cy[9]), .I2(1'b1), .I1(1'b0), .I0(load));
SB_CARRY msbcy( .CO(cy[10]), .CI(cy[9]), .I1(1'b1), .I0(1'b0));
SB_DFFE txbusy_r( .Q(txbusy), .C(clk), .E(load0Rtxce), .D(c_txbusy));

```

Finally we have the synchronisation stage. $pp \leftarrow load * pp \mid \sim load * txce \& cy_{10} * a_0 \mid \sim load \& \sim txce \& pp$ is implemented.

6b $\langle ll \text{ uarttx module code 4b} \rangle + \equiv$ (14b) $\triangleleft 6a$

```

SB_LUT4 #(.LUT_INIT(16'hb888))
pp_i( .O(c_pp), .I3(cy[10]), .I2(a[0]), .I1(load), .I0(txpin));
SB_DFFE pp_r( .Q(txpin), .C(clk), .E(load0Rtxce), .D(c_pp) );
endmodule

```

Receive module

4.1 High level implementation

The receive module consists of a receive state machine and a receive shift register. See page 8 for the receive state machine.

```
7  <hl uartrx module 7>≡ (14a)
    module uartrx_m
        # (parameter HUNT = 2'b00, GRCE = 2'b01, ARMD = 2'b10, RECV = 2'b11 )
        (
            input          clk,rxce,rxpin,
            output         bytercvd,
            output [1:0]   rxst,
            output reg [7:0] q
        );
        uartrxsm_m #(.HUNT(HUNT), .GRCE(GRCE), .ARMD(ARMD), .RECV(RECV))
        rxsm(// Inputs
            .lastbit( q[0] ),
            /*AUTOINST*/);
        always @(posedge clk)
            if ( rxce )
                q <= (rxst == ARMD) ? 8'h80 : (rxst == RECV) ? {rxpin,q[7:1]} : q;
    endmodule
```

Each rxce, if the state machine is in state ARMD, the shift register is initiated to 8'h80. If we are receiving, the shift register is shifted. Otherwise the shift register is held.

By initiating the shift register to 8'h80, we know a complete byte is received when a 1'b1 is shifted out of the shift register, so we need no counter for the number of received bits.

High level receive state machine

The states of the state machine is encoded as parameters to avoid polluting the name space. When rxce is active (in general 8 or 16 times per bit), the state machine may change state. But note that rxce is active every cycle when the state machine is in states GRCE and HUNT.

```

8  <hl uartrx state machine module 8>≡ (14a)
    module uartrxsm_m
        # ( parameter HUNT = 2'b00, GRCE = 2'b01, ARMD = 2'b10, RECV = 2'b11 )
        (input          clk,rxce,rxpin,lastbit,
         output         bytercvd,
         output reg [1:0] rxst
        );
        reg [1:0]      nxt;
        always @(*AS*/) begin
            casez ( {rxst,rxpin,lastbit,rxce} )
                {HUNT,3'b1??} : nxt = HUNT;
                {HUNT,3'b0?0} : nxt = HUNT;
                {HUNT,3'b0?1} : nxt = ARMD;
                {ARMD,3'b??0} : nxt = ARMD;
                {ARMD,3'b0?1} : nxt = RECV;
                {ARMD,3'b1?1} : nxt = HUNT; // False start bit.
                {RECV,3'b??0} : nxt = RECV;
                {RECV,3'b?01} : nxt = RECV;
                {RECV,3'b?11} : nxt = GRCE;
                {GRCE,3'b??0} : nxt = GRCE;
                {GRCE,3'b0?1} : nxt = HUNT; // Stop bit wrong, reject byte.
                {GRCE,3'b1?1} : nxt = HUNT; // Byte received
            endcase
        end
        always @(posedge clk)
            rxst <= nxt;
        assign bytercvd = (rxst == GRCE) && rxpin && rxce;
    endmodule

```

When hunting for a start bit (HUNT), if the rxpin is low, the state machine transitions into the armed state (ARMD). After 1/2 bit time, rxpin is resampled. If it is low, we conclude a start bit has been seen. If the input is noisy, this is likely to be a bad implementation, but easily corrected by applying a digital low-pass filter on the rxpin.

After the last data bit has been sampled, we need a way to get back to HUNT for the next byte. We can not go directly to HUNT because we are in the middle of the last data bit, which may very well be a 1'b0, and would be mistaken for the start of a start bit. There are several ways to handle this situation.

- We can stupidly sample one more bit, it should be high (the frame bit), and we then give an information of a failed frame bit if it turns out to be low.
- We can change how we detect the start of a start bit, and demand a high to low transition on the receive line.

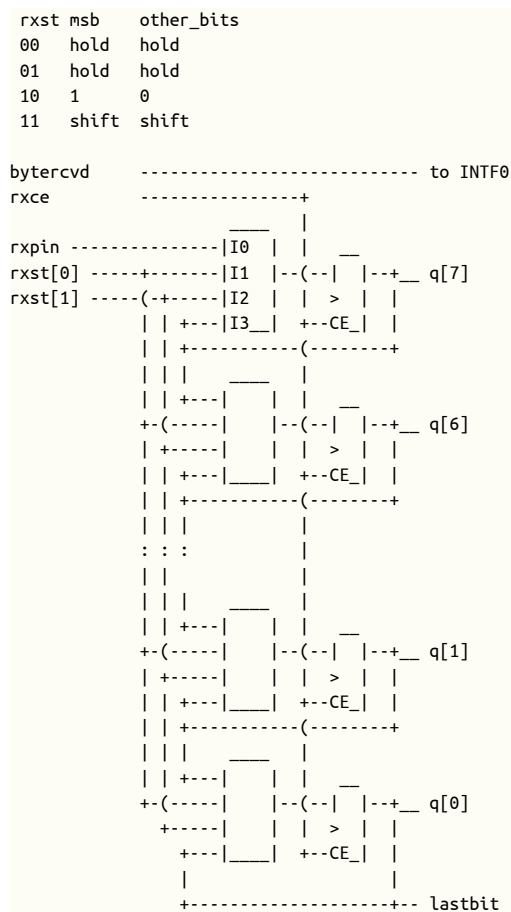


Figure 4.1: Small sketch of receive shift register

- We can go to a state GRCE after sampling the last data bit, and change how we generate rxce. If we generate rxce each clock cycle we are in state GRCE and monitor the receive line, we can go to state HUNT when we see a transition on the receive line to 1'b1.

We do the last, with an added twist – rxce will only be high when we are in state HUNT if rxpin is high. This implies that as long as a faulty stop bit lies low, we will not get to state ARMD.

After the last data bit has been sampled, the state machine goes to GRCE. The bitclock divider unit know when the receive state machine is in GRCE, and if it sees a high data bit, it will give a rxce, this will then lead to a quicker entry to the HUNT state. This way to treat the stop bit is very permissive. A few cycles of stop bit is all that is needed to put the receiver state machine on its tracks again. A possible disadvantage is that the rxpin will be accessed in two consecutive clock cycles just when a stop bit starts (in case d[7] was low), and on a noisy line this may then give a false start bit. If this becomes an identified problem, we should implement a digital low-pass filter in front of the uart.

4.2 Low level implementation

A low level version of the state machine need only three LUTs.

10a (14b)

```

<ll uartrx state machine module 10a>≡
module uartrxsm_m
  (input      clk,rxce,rxpin,lastbit,
   output     bytercvd,
   output [1:0] rxst
  );
  wire [1:0]  nxt_rxst;

  SB_LUT4 #(.LUT_INIT(16'h5303))
  stnxt1_i( .O(nxt_rxst[1]),.I3(rxst[1]),.I2(rxst[0]),.I1(rxpín),.I0(lastbit));
  SB_LUT4 #(.LUT_INIT(16'hf300))
  stnxt0_i( .O(nxt_rxst[0]), .I3(rxst[1]), .I2(rxst[0]), .I1(rxpín),.I0(1'b0));
  SB_DFFE r_st0( .Q(rxst[0]), .C(clk), .E(rxce), .D(nxt_rxst[0]));
  SB_DFFE r_st1( .Q(rxst[1]), .C(clk), .E(rxce), .D(nxt_rxst[1]));
  SB_LUT4 #(.LUT_INIT(16'h0080))
  bytercvd_i( .O(bytercvd), .I3(rxst[1]), .I2(rxst[0]), .I1(rxpín), .I0(rxce));
endmodule

```

The receive state machine is assembled with the shift register, implemented in a generate loop.
Total size 11 logicCells.

10b (14b) 10c▷

```

<ll uartrx module 10b>≡
module uartrx_m
  (
   input      clk,rxce,rxpin,
   output     bytercvd,
   output [1:0] rxst,
   output [7:0] q
  );
  genvar      i;
  wire [7:0]  c_sh;

```

10c (14b) ◁10b

```

<ll uartrx module 10b>+≡
  uartrxsm_m rxsm(// Inputs
                  .lastbit( q[0] ),
                  /*AUTOINST*/);

  generate
    for ( i = 0; i < 8; i = i + 1 ) begin : blk
      localparam a = i == 7 ? 16'hbfb0 : 16'h8f80;
      SB_LUT4 #(.LUT_INIT(a))
      sh( .O(c_sh[i]), .I3(q[i]), .I2(rxst[1]), .I1(rxst[0]),
          .I0(i==7 ? rxpin:q[i+1]));
      SB_DFFE shreg( .Q(q[i]), .C(clk), .E(rxce), .D(c_sh[i]) );
    end
  endgenerate
endmodule

```

The dividers

An important input to the uart is the `bitxce` clock. It is used to increment a free-running 3 or 4 bit counter destined for the transmit module. It is also used to increment a 3 or 4 bit resettable counter destined for the receive module.

When the transmission rate of the uart is close to `clk/8` (or `clk/16`), we reset the `rxce` counter to 5 (or 9) rather than to 4 (or 8). This fine-adjustment places sampling of bits closer to the middle of the window in these cases.

5.1 High level implementation

```

11  <hl uart counters module 11>≡ (14a)
    module rtxdiv_m
      # (parameter HUNT = 2'b00, GRCE = 2'b01, ARMD = 2'b10, RECV = 2'b11,
        SUBDIV16 = 0, ADJUSTSAMPLEPOINT = 0
      )
      (input      clk,bitxce,load,rxpin,
       input [1:0] rxst,
       output     loadORtxce,
       output reg  rxce
      );
      localparam rstval = SUBDIV16 ? (ADJUSTSAMPLEPOINT ? 4'b1001 : 4'b1000) :
        (ADJUSTSAMPLEPOINT ? 3'b101 : 3'b100);
      reg [2+SUBDIV16:0] txcnt,rxcnt;
      always @(posedge clk) begin
        if ( bitxce ) begin
          txcnt <= txcnt + 1;
          rxcnt <= rxst == HUNT ? rstval : (rxcnt+1);
        end
        rxce <= ((rxst != HUNT) & (&rxcnt & bitxce) )
          | ((rxst == HUNT | rxst == GRCE) & rxpin);
      end
      assign loadORtxce = (&txcnt & bitxce) | load;
    endmodule

```

5.2 Low level implementation

A sketch of the implementation (in 9 or 11 logicCells) is seen in figure 5.1.

```

12  <ll uart counters module 12>≡ (14b)
    module rtxdiv_m
        #( parameter ADJUSTSAMPLEPOINT = 0, SUBDIV16 = 0)
        (input      clk,bitxce,load,rxpin,
         input [1:0] rxst,
         output      load0Rtxce,rxce
         );
        localparam rstval_lsb = ADJUSTSAMPLEPOINT ? 16'haffa : 16'h0550;
        localparam LOOPLIM = SUBDIV16 ? 4 : 3;
        wire [LOOPLIM+1:0] cy,rxcy;
        wire      c_rxce,rst4;
        wire [LOOPLIM-1:0] c_txcnt,txcnt,c_rxcnt,rxcnt;
        genvar      j;

        assign cy[0] = 1'b0;
        generate
            for ( j = 0; j < LOOPLIM; j = j + 1 ) begin : blk0
                SB_LUT4 #(.LUT_INIT(16'hc33c)) i_txcnt1(.0(c_txcnt[j]),
                    .I3(cy[j]), .I2(txcnt[j]), .I1(j==0 ? bitxce:1'b0), .I0(1'b0));
                SB_CARRY i_cy1(.CO(cy[j+1]),
                    .CI(cy[j]), .I1(txcnt[j]), .I0(j==0 ? bitxce:1'b0));
                SB_DFF reg1( .Q(txcnt[j]), .C(clk), .D(c_txcnt[j]));
                if ( j == LOOPLIM-1 ) begin
                    SB_LUT4 #(.LUT_INIT(16'hfaaa))
                        i_txcnt3(.0(load0Rtxce),
                            .I3(cy[j+1]),.I2(bitxce ), .I1(bitxce),.I0(load));
                    SB_CARRY i_cy3(.CO(rxcy[0]),
                        .CI(cy[j+1]),.I1(bitxce ), .I0(bitxce));
                end
            end
        endgenerate
        generate
            for ( j = 0; j < LOOPLIM; j = j + 1 ) begin : blk1
                if ( j != LOOPLIM-1 ) begin
                    SB_LUT4 #(.LUT_INIT(j == 0 ? rstval_lsb : 16'h0550)) i_rxcnt0
                        (.0(c_rxcnt[j]), .I3(rxcy[j]), .I2(rxcnt[j]),.I1(1'b0),.I0(rst4));
                    SB_CARRY i_cy4(.CO(rxcy[j+1]),.CI(rxcy[j]),.I1(rxcnt[j]),.I0(1'b0));
                end else begin
                    SB_LUT4 #(.LUT_INIT(j == (LOOPLIM-1) ? 16'hcffc:16'h0550)) i_rxcntl
                        (.0(c_rxcnt[j]), .I3(rxcy[j]), .I2(rxcnt[j]),.I1(rst4),.I0(1'b0));
                    SB_CARRY i_cy4(.CO(rxcy[j+1]),.CI(rxcy[j]),.I1(rxcnt[j]),.I0(rst4));
                end
                SB_DFF reg4( .Q(rxcnt[j]), .C(clk), .D(c_rxcnt[j]));
                if ( j == LOOPLIM-1 ) begin
                    SB_LUT4 #(.LUT_INIT(16'h0055)) i_rst
                        (.0(rst4), .I3(rxst[1]), .I2(1'b0),.I1(bitxce), .I0(rxst[0]));
                    SB_CARRY i_andcy
                        (.CO(rxcy[j+2]),.CI(rxcy[j+1]),.I1(1'b0),.I0(bitxce));
                    SB_LUT4 #(.LUT_INIT(16'hfe30)) i_rxce
                        (.0(c_rxce), .I3(rxcy[j+2]),.I2(rxpin),.I1(rxst[1]),.I0(rxst[0]));
                    SB_DFF regrxce( .Q(rxce), .C(clk), .D(c_rxce));
                end
            end
        endgenerate
    endmodule

```

```

rxstate[0] --| I0 | __
rxstate[1] --| I1 | -| | - rxce = (rxcy & bitxce & (!HUNT) ) |
rxpin -----| I2 | >__| (GRCE | HUNT) & rxpin
+-----| I3 |
|
| rxcy & bitxce "(receive count overflow, or rst4) & bitxce"
/cy\
rxst[0](((---- I0 rst4 = rxst == 2'b0
bitxce ---+((---- I1 Note that carry is not entered into
0 ----(+--- I2 this LUT, but it could be, can move
rxst[1]-(--- I3 rxst[1] to I2.
|
/cy\
0 -(((---- I0 rxcnt is an up-counter
rst4 --+((---- I1 ~rst4&(rxcnt2^cy) ---| |-- rxcnt2
rxcnt2 --(+---- I2 | rst4 >__|
+----- I3
|
/cy\
rst4-(((---- I0
0 --+((---- I1 ~rst4&(rxcnt1^cy) ---| |-- rxcnt1
rxcnt1 --(+---- I2 >__|
+----- I3
|
/cy\
rst4-(((---- I0
0 --+((---- I1 ~rst4&(rxcnt0^bitxce) ---| |-- rxcnt0
rxcnt0 --(+---- I2 >__|
+----- I3
| bitxce
/cy\
load -(((---- I0
bitxce --+((---- I1
bitxce --(+---- I2 (cy&bitxce) | load = load0Rtxce
+----- I3
|
/cy\
0 -(((---- I0 txcnt is a up-counter
0 --+((---- I1 (bitxce^txcnt2^cy)---| |-- txcnt2
txcnt2 --(+---- I2 >__|
+----- I3
|
/cy\
0 -(((---- I0
0 --+((---- I1 (bitxce^txcnt1^cy)---| |-- txcnt1
txcnt1 --(+---- I2 >__|
+----- I3
|
/cy\
0 -(((---- I0
bitxce --+((---- I1 (bitxce^txcnt0^0) ---| |-- txcnt0
txcnt0 --(+---- I2 >__|
+----- I3
|
gnd

```

Figure 5.1: Approximative sketch of counters for uart control

All together

6.1 High level implementation

```
14a <../src/uartICE40hl.v 14a>≡
    /* High level version of a small simple asynchronous transmitter/receiver
       For documentation see the wiki pages. */
    <module head 2a>
    <module body 2b>
    <hl uarttx module 3>
    <hl uartrx state machine module 8>
    <hl uartrx module 7>
    <hl uart counters module 11>
```

6.2 Low level implementation

Total size is $12+11+9 = 32$ logicCells when we oversample 8 times, and $12+11+11 = 34$ logicCells when we oversample 16 times.

```
14b <../src/uartICE40.v 14b>≡
    /* A small simple asynchronous transmitter/receiver
       For documentation see the wiki pages. */
    <module head 2a>
    <module body 2b>
    <ll uarttx module head 4a>
    <ll uarttx module code 4b>
    <ll uartrx state machine module 10a>
    <ll uartrx module 10b>
    <ll uart counters module 12>
```

Testbench

A previous implementation of the uart generated the x8 (or x16) bit clock internal to the module. This complicated simulation. Now that the important `bitxce` input is external to the uart, testing is simplified.

7.1 What do we test?

Two instances of `uartICE40` are used, one for tx and one for rx. Transmission of a byte with lsb set to 0, and transmission of a byte with lsb set to 1 is tested first. Then test recovery of the receive unit in case of a glitch (false startbit). Finally we test that a byte where the frame bit is missing is rejected.

We do the tests both for a constantly active `txce/rxce` and for `txce/rxce` active one in 8 cycles. We do this for both the high level, and the low level code.

7.2 Test bench proper

```
15  <../src/tbuartICE40.v 15>≡ 16a▷
    module tst;
        reg [31:0] cyclecounter,simtocy,tx_cyclecounter;
        reg      load,bytercvd_dly1;
        wire      rxpin;
        reg [7:0] d;
        reg      seenB;
        reg      base_clk;
        reg      rx_clk;
        reg      tx_clk;
        reg [2:0] bitxce_tx_cnt;
        reg [2:0] bitxce_rx_cnt;
        reg      glitchline,check_rxst1;
        localparam char1 = 8'hc1, char2 = 8'h4e;
        localparam SIMTOCY = 100 + 2*8*8*8*10*(1+'SUBDIV16);
        localparam RXCLKSTART = 100;
        localparam subdiv16 = 'SUBDIV16; // From makefile
```

We want to instantiate two uarts, one for transmit and one for receive. We then send a character 8'hc1, followed by 8'h4e. Lets start by defining a base clock, and do some initiation:

```
16a <./src/tbuartICE40.v 15>+≡ <15 16b>
/*AUTOWIRE*/
always # 20 base_clk = ~base_clk;

initial begin
    $dumpfile('TSTFILE');//obj/tst.lxt"
    $dumpvars(0,tst);
    d <= 0;      tx_clk <= 0;      simtocy = SIMTOCY;  bitxce_rx_cnt <= 0;
    load <= 0;   rx_clk <= 0;      cyclecounter <= 0;  tx_cyclecounter <= 0;
    seenB <= 0;  base_clk <= 0;    bitxce_tx_cnt <= 0;
    check_rxst1 <= 0;             glitchline <= 0;
end
```

We should have a result in not too many cycles:

```
16b <./src/tbuartICE40.v 15>+≡ <16a 16c>
always @(posedge base_clk ) begin
    cyclecounter <= cyclecounter+1;
    if ( cyclecounter > SIMTOCY ) begin
        if ( simtocy == SIMTOCY )
            $display( "Simulation went off the rails" );
        else
            $display( "Success" );
        $finish;
    end
    tx_clk <= ~tx_clk;
    if ( cyclecounter > RXCLKSTART )
        rx_clk <= ~rx_clk;
end
```

Feed the transmitting uart.

```
16c <./src/tbuartICE40.v 15>+≡ <16b 16d>
always @(posedge tx_clk) begin
    tx_cyclecounter <= tx_cyclecounter + 1;
    load <= ( tx_cyclecounter == 100 ||
              tx_cyclecounter == 100 + 8*8*10*(1+'SUBDIV16) ||
              tx_cyclecounter == 100 + 3*8*8*10*(1+'SUBDIV16) )
            ? 1'b1 : 1'b0;
```

Clumsily present characters to the transmit unit

```
16d <./src/tbuartICE40.v 15>+≡ <16c 17a>
if ( tx_cyclecounter == 99 ) begin
    d <= char1;
end else if ( tx_cyclecounter == 150 ) begin
    d <= char2;
end
```

At a certain time, glitch the line to introduce a false start bit. We also let the line be low to introduce an erroneous frame bit.

```
17a  <../src/tbuartICE40.v 15>+≡ <16d 17b>
      if ( ( tx_cyclecounter >= 100 + 2*8*8*10*(1+'SUBDIV16) &&
            tx_cyclecounter <= 103 + 2*8*8*10*(1+'SUBDIV16) )
        || ( tx_cyclecounter >= 100 + 4*8*8*10*(1+'SUBDIV16)
            - 64*(1+'SUBDIV16) &&
            tx_cyclecounter <= 100 + 4*8*8*10*(1+'SUBDIV16)
            + 64*(1+'SUBDIV16) + 2*64 ) )
        glitchline <= 1'b1;
      else
        glitchline <= 1'b0;
```

A rather weak test to see that the receive unit is in state HUNT after rejecting a false start bit. We check this in the tx clock domain. A similarly weak test to see that we end up in HUNT after rejecting a byte.

```
17b  <../src/tbuartICE40.v 15>+≡ <17a 18a>
      if ( tx_cyclecounter == 100 + 2*8*8*10*(1+'SUBDIV16)
        + 4*8*(1+'SUBDIV16) ||
        tx_cyclecounter >= 100 + 4*8*8*10*(1+'SUBDIV16)
        + 64*(1+'SUBDIV16) + 2*64 )
      begin
        check_rxst1 <= 1;
        if ( rxst != 2'b00 ) // Encoding of HUNT is 2'b00.
        begin
          if (tx_cyclecounter == 100 + 2*8*8*10*(1+'SUBDIV16)
            + 4*8*(1+'SUBDIV16))
            $display( "False start bit not rejected" );
          else
            $display( "Something wrong at frame error" );
          $finish;
        end
      end else begin
        check_rxst1 <= 0;
      end
    end
```


For the receiver:

```
19a <../src/tbuartICE40.v 15>+≡ <18b 19b>
    uartICE40
    #( .SUBDIV16(subdiv16), .ADJUSTSAMPLEPOINT(adjsamplept))
    dut_rx
    (// Outputs
      .txpin( dummy_txpin ),
      .txbusy( dummy_txbusy ),
      // Inputs
      .clk (rx_clk ),
      .bitxce(bitxce_rx),
      .load( 1'b0 ),
      .d (0),
      /*AUTOINST*/);
```

I also want to simulate a false start bit. This I do by suitably glitch the line at the top level. The testbench uses a bit-serial loopback. Pads not simulated, so txpin inverted here.

```
19b <../src/tbuartICE40.v 15>+≡ <19a 19c>
    assign rxpin = ~txpin & ~glitchline;
```

Provide the 8 or 16 times bitrate clocks:

```
19c <../src/tbuartICE40.v 15>+≡ <19b>
    always @(posedge tx_clk)
        bitxce_tx_cnt <= bitxce_tx_cnt + 1;
    always @(posedge rx_clk)
        bitxce_rx_cnt <= bitxce_rx_cnt + 1;
    assign bitxce_tx = bitxce_tx_cnt == 0 || 'BITLAX;
    assign bitxce_rx = bitxce_rx_cnt == 0 || 'BITLAX;
endmodule
```

7.3 Use of the test bench

I tested the module using the excellent `iverilog/gtkwave` combination, with a scruffy home-grown simulation library. No attempt is made to provide these elements to other readers. I recommend any users of `uartICE40` to do their own testing, in their own environment. The testbench above could be used as a starting point.

Tested

8 variants are tested. Only a few are really well tested, more work, but not now.

tst00.ltx	High-level code	8-times oversampling	bitxce active one of 8 cycles
tst01.ltx	High-level code	8-times oversampling	bitxce active each cycle
tst10.ltx	High-level code	16-times oversampling	bitxce active one of 8 cycles
tst11.ltx	High-level code	16-times oversampling	bitxce active each cycle
ltst00.ltx	Low-level code	8-times oversampling	bitxce active one of 8 cycles
ltst01.ltx	Low-level code	8-times oversampling	bitxce active each cycle
ltst10.ltx	Low-level code	16-times oversampling	bitxce active one of 8 cycles
ltst11.ltx	Low-level code	16-times oversampling	bitxce active each cycle

ICEstick

A top level module is needed for a rudimentary synthesis. This design implements an UART in loopback. Several of the LEDs of the ICEstick are not connected, and will flicker.

```
20a <../src/icestickuart.v 20a>≡ 20b▷
/* Top level that just instantiates a UART in loopback mode in an icestick.
 * Assumptions: 12M clock. 115200 bps. 8N1 format.
 * Note: Needs retesting on hardware after code reorganization.
 */
/*
 * LogicCells:
 * 38 for uart proper
 * 1 for metastability removal rxpin
 * 1 for generation of constant 1'b1.
 * ---
 * 40 logicCells in total
 */
/*
PIO3_08 _ rxpinmeta1 _| _| _ rxpin -> UART
[x] --| |>_| |>_|
UART - txpin ->| |>|>o-[x] PIO03_07
>_|
*/
```

Unconfirmed: It seems that yosys has an error that means that the signal at the top level, connected input signal, (these instantiated as input pins by SB_IO) must be named as input only.

```
20b <../src/icestickuart.v 20a>+≡ <20a 21a>
module top
// ( inout PIO3_08,PIO3_07,PIO1_14,PIO1_02,GBIN6
// );
( input PIO3_08, GBIN6,
output PIO3_07, PIO1_14, PIO1_02
);
wire [7:0] d;
wire clk,cte1,rxpinmeta1,c_rxpinmeta1,rxpin;
reg [4:0] bitxcent;
/*AUTOWIRE*/
```

One LUT is consumed to get a constant 1. A trick to save a LUT would be to get constant 1 from an unbonded pad instead.

21a `<../src/icestickuart.v 20a>+≡` `assign cte1 = 1'b1;` `<20b 21b>`

Then follows the pin instantiations

21b `<../src/icestickuart.v 20a>+≡` `<21a 21c>`

```
// Clock pin
SB_GB_IO clockpin
( .PACKAGE_PIN(GBIN6), .GLOBAL_BUFFER_OUTPUT(clk));

// Transmit pin
SB_IO #( .PIN_TYPE(6'b011111)) // OUTPUT_REGISTERED/INPUT_LATCH
IO_tx ( .PACKAGE_PIN(PIO3_07), .OUTPUT_CLK(clk), .D_OUT_0(txpin) );

// txbusy to LED0
SB_IO #( .PIN_TYPE(6'b010111)) // OUTPUT_REGISTERED/INPUT_LATCH
IO_txbusy ( .PACKAGE_PIN(PIO1_14), .OUTPUT_CLK(clk), .D_OUT_0(txbusy) );

// bitxce to J2 pin 1 for debugging
SB_IO #( .PIN_TYPE(6'b010111)) // OUTPUT_REGISTERED/INPUT_LATCH
IO_bitxce ( .PACKAGE_PIN(PIO1_02), .OUTPUT_CLK(clk), .D_OUT_0(bitxce) );

// Receive pin
SB_IO #( .PIN_TYPE(6'b000000)) // NO_OUTPUT/INPUT_REGISTERED
IO_rx ( .PACKAGE_PIN(PIO3_08), .INPUT_CLK(clk), .D_IN_0(rxpinmeta1) );
```

Metastability reduction. I explicitly instantiate a LUT:

21c `<../src/icestickuart.v 20a>+≡` `<21b 21d>`

```
SB_LUT4 #( .LUT_INIT(16'haaaa))
cmb( .O(c_rxpinmeta1), .I3(1'b0), .I2(1'b0), .I1(1'b0), .IO(rxpinmeta1));
SB_DFF metareg( .Q(rxpin), .C(clk), .D(c_rxpinmeta1));
```

We assume to have a 12 MHz clock, and want a bitrate of 115200. Hence we need a prescaler $\frac{12000000}{115200 \times 8} = 13.02$ The easiest way I can think of, is a 5-bit counter that counts the sequence

`4 5 6 7 8 9 0xa 0xb 0xc 0xd 0xe 0xf 0x10`.

21d `<../src/icestickuart.v 20a>+≡` `<21c>`

```
always @(posedge clk)
    bitxcecnt <= bitxcecnt[4] ? 5'h4 : bitxcecnt+5'h1;
assign bitxce = bitxcecnt[4];
// The module proper
uartICE40 uart
(*AUTOINST*);

// Connect the uart in loopback:
assign load = bytercvd;
assign d = q;
endmodule

// Local Variables:
// verilog-library-directories:(" " ../fromrefdesign/ )
// verilog-library-files:(".././../PROJ/iCE_simlib/iCE_simlib.v" "uart.v" )
// verilog-library-extensions:(".v" )
// End:
```

8.1 Compilation results

8.1.1 Synplify, low level

When using the low level implementation, the following excerpt from the “placer.log” file show the size:

```
Input Design Statistics
  Number of LUTs      :      38
  Number of DFFs      :      35
  Number of Carrys    :      21
  Number of RAMs      :       0
  Number of ROMs      :       0
  Number of IOs       :       4
  Number of GBIOs     :       1
  Number of GBs       :       0
  Number of WarmBoot  :       0
  Number of PLLs      :       0

..snip..
Final Design Statistics
  Number of LUTs      :      39
  Number of DFFs      :      35
  Number of Carrys    :      21
  Number of RAMs      :       0
  Number of ROMs      :       0
  Number of IOs       :       4
  Number of GBIOs     :       1
  Number of GBs       :       0
  Number of WarmBoot  :       0
  Number of PLLs      :       0

Device Utilization Summary
  LogicCells          :      41/1280
  PLBs                :       9/160
  BRAMs               :       0/16
  IOs and GBIOs       :       5/96
  PLLs                :       0/1
```

This was when compiling with Synplify. Design resource usage is theoretically:

32	Uart proper
5	Predivider
1	Removal of metastability from rxpin
1	Generation of constant 1'b1
<hr/>	
39	Total

This matches the real result.

8.1.2 Synplify, high level

The same exercise for the high-level implementation, copy-paste of pieces of “placer.log”:

I2053: Starting placement of the design

```
=====

Input Design Statistics
  Number of LUTs           :    38
  Number of DFFs           :    35
  Number of Carrys         :     3
  Number of RAMs           :     0
  Number of ROMs           :     0
  Number of IOs            :     4
  Number of GBIOs          :     1
  Number of GBs            :     0
  Number of WarmBoot       :     0
  Number of PLLs           :     0

Phase 1
I2077: Start design legalization

Design Legalization Statistics
  Number of feedthru LUTs inserted to legalize input of DFFs      :     8
  Number of feedthru LUTs inserted for LUTs driving multiple DFFs :     0
  Number of LUTs replicated for LUTs driving multiple DFFs       :     1
  Number of feedthru LUTs inserted to legalize output of CARRYs   :     0
  Number of feedthru LUTs inserted to legalize global signals      :     0
  Number of feedthru CARRYs inserted to legalize input of CARRYs  :     0
  Number of inserted LUTs to Legalize IOs with PIN_TYPE= 01xxxx   :     0
  Number of inserted LUTs to Legalize IOs with PIN_TYPE= 10xxxx   :     0
  Number of inserted LUTs to Legalize IOs with PIN_TYPE= 11xxxx   :     0
  Total LUTs inserted                                              :     9
  Total CARRYs inserted                                           :     0
..snip..

Final Design Statistics
  Number of LUTs           :    47
  Number of DFFs           :    35
  Number of Carrys         :     3
  Number of RAMs           :     0
  Number of ROMs           :     0
  Number of IOs            :     4
  Number of GBIOs          :     1
  Number of GBs            :     0
  Number of WarmBoot       :     0
  Number of PLLs           :     0

Device Utilization Summary
  LogicCells               :    48/1280
  PLBs                     :     8/160
  BRAMs                   :     0/16
  IOs and GBIOs           :     5/96
  PLLs                     :     0/1
```

I2076: Placer run-time: 11.4 sec.

Note that few carry-chain resources are used above. The high-level implementation use LUTs to find out if the transmit buffer is empty.

Conclusion

The low level implementation uses 32 logicCells, while the high level implementation uses 39 logicCells. This is a lot of effort (and user unfriendly code) for a meagre saving of 7 logicCells. If I had been able to write a good high-level module from the very start, a lot of effort had been saved. However, the high-level module was made *after* the low-level module, and reflects the design choices of the low-level module. A conclusion must be: Think low-level, code high-level.

And this ends the documentation of a simulated and tested small asynchronous receiver/transmitter specifically written for iCE40 FPGAs.